

## The RLC Circuit

A circuit with a resistor, an inductor, and a capacitor connected in series, commonly called an RLC circuit, is described by the following differential equation,

$$LQ'' + RQ' + Q/C = V(t) \quad (1)$$

where  $Q$  is the charge ( $Q'$  being the current),  $L$  is the inductance of the inductor,  $R$  is the resistance of the resistor,  $C$  is the capacitance of the capacitor, and  $V(t)$  is a time dependent driving voltage. Note the striking similarity to the damped spring differential equation,

$$mx'' + cx' + kx = F(t) \quad (1')$$

where  $x$  is the position,  $m$  is the mass,  $c$  is the damping constant,  $k$  is the spring constant, and  $F(t)$  is a time dependent applied force. Remember the same equations have the same solutions, regardless of what you call the variables involved.

Assuming a sinusoidal driving voltage of the form  $V(t) = V_0 \sin \omega t$  yields

$$LQ'' + RQ' + Q/C = V_0 \sin \omega t \quad (2)$$

and differentiating

$$LI'' + RI' + I/C = \omega V_0 \cos \omega t \quad (3)$$

where  $I$ , of course, is the current. The solution to (3) will be a sum of two parts, the homogeneous solution  $I_h(t)$  and the non-homogeneous solution  $I_{osc}(t)$ . Solving the characteristic equation

$$Lr^2 + Rr + 1/C = 0 \quad (4)$$

yields roots

$$r = \frac{-R \pm \sqrt{R^2 - 4L/C}}{2L} \quad (5)$$


which leads to three cases (the nomenclature is in analogy to the damped spring):

### 1. **Overdamped** ( $R^2 > 4L/C$ )

For this case the characteristic equation has two distinct negative real roots  $-\alpha$  and  $-\beta$  yielding the homogeneous solution

$$I_h(t) = c_1 e^{-\alpha t} + c_2 e^{-\beta t} \quad (6)$$

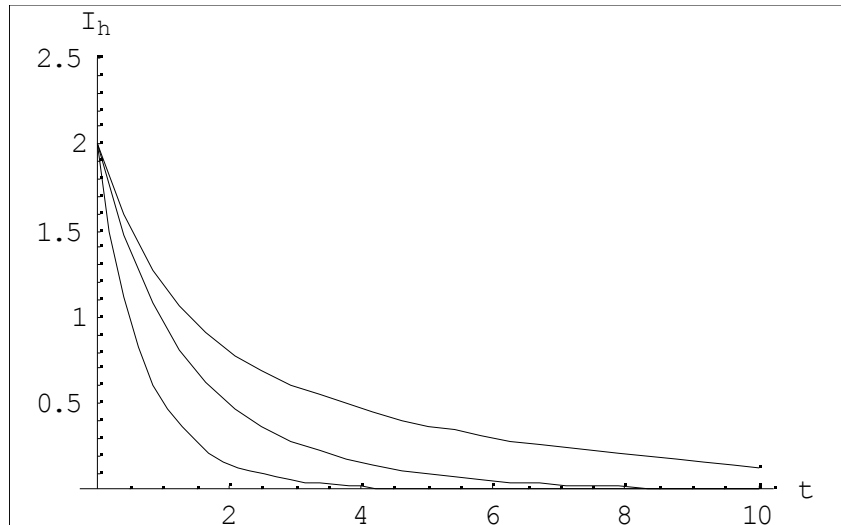where  $c_1$  and  $c_2$  are arbitrary constants. Below are several plots of this solution for various values of the constants.




## 2. Critically damped ( $R^2 = 4L/C$ )

For this case the characteristic equation has a single distinct negative real root  $-r$  yielding the homogeneous solution

$$I_h(t) = e^{-rt}(c_1 + c_2 t) \quad (7)$$

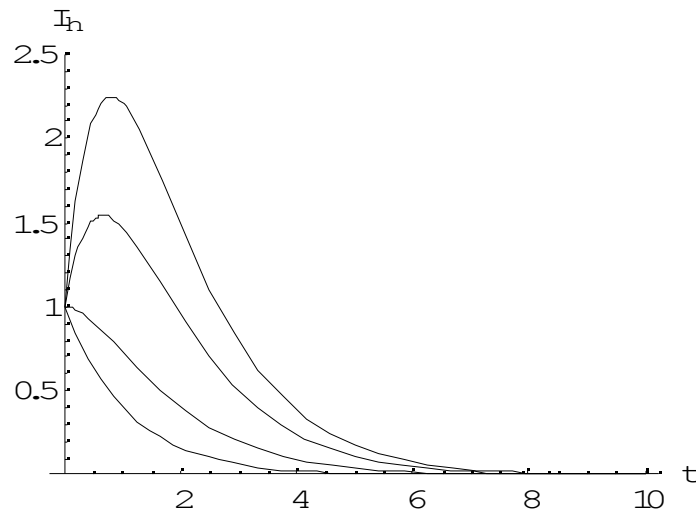where  $c_1$  and  $c_2$  are arbitrary constants. Below are four plots of this solution for different choices of constants.




## 3. Underdamped ( $R^2 < 4L/C$ )

For this case the characteristic equation has two distinct complex roots  $-r \pm \gamma i$  yielding the homogeneous solution

$$I_h(t) = e^{-rt}(c_1 \cos \gamma t + c_2 \sin \gamma t) \quad (8)$$

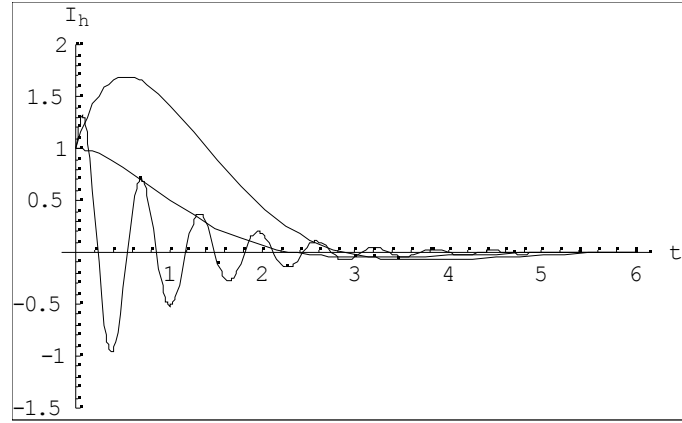where  $c_1$  and  $c_2$  are arbitrary constants. Below are several plots of the solution with various constants.



Looking at these three possibilities it is clear that  $I_h(t)$  will die off in any case leaving  $I(t) \approx I_{osc}(t)$  after some finite time. Using the method of undetermined coefficients we find the non-homogeneous solution to be

$$I_{osc}(t) = I_0 \cos(\omega t - \phi) \quad (9)$$

where  $I_0 = V_0 / \sqrt{R^2 + (\omega L - 1/\omega C)^2}$  and  $\phi = \tan^{-1} \omega RC / (1 - LC\omega^2)$ . The quantity in the denominator

$$Z = \sqrt{R^2 + (\omega L - 1/\omega C)^2} \quad (10)$$

is commonly called the impedance. Note that the amplitude of  $I_{osc}(t)$  is

$$I_0 = V_0 / Z \quad (11)$$

which should remind you of Ohm's Law, with  $Z$  as a coefficient that describes how a given circuit *impedes* the flow of current. It should not be surprising that the units of  $Z$  are Ohms  $[\Omega]$ . Furthermore, there is also a special name for the the quantity in parentheses,


$$S = \omega L - 1/\omega C \quad (12)$$

the reactance, which also has units  $[\Omega]$ . This quantity tells you how a given circuit *reacts* to a certain frequency driving voltage.

Now if we look at  $I_0$  as a function of  $\omega$  (pictured below), it is clear that to maximize this amplitude we must have  $S = 0$ , or

$$\omega_R = (LC)^{-1/2} \quad (13)$$

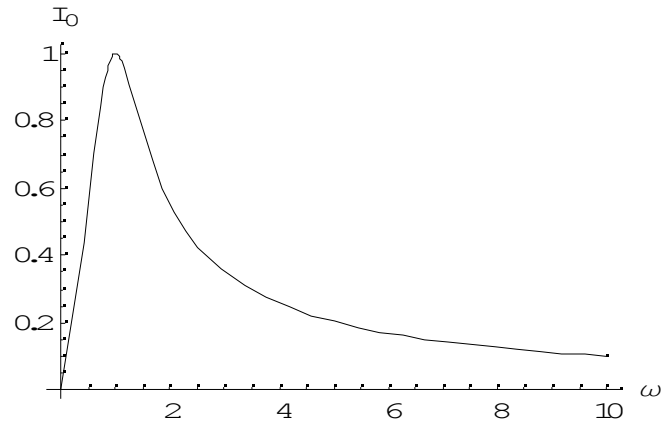so that  $Z = R$ . This frequency,  $\omega_R$ , is called the resonant frequency.



### References:

Edwards, C.H. Jr. and David E. Penney, *Differential Equations: Computing and Modeling*, Ch. 3 (1996).

The graphs were produced using *Mathematica*.